 


- 1 Consider the following circuit of priority encoder. What is the correct priority order of the input lines? 1 point



- ☐ D1>D2>D0>D3
☐ D2>D1>D3>D0
☒ D2>D0>D1>D3
☐ D3>D1>D0>D2

Clear selection

- 2 The POS form for the function $f(A,B,C,D) = \sum m(0,2,4,8,10,14)$ is 1 point

- ☒ $D'(A+B'+C')(A'+B'+C)$
☐ $D'(A+B'+C)(A'+B'+C)$
☐ $D'(A+B'+C')(A'+B+C)$
☐ $D'(A+B'+C)(A+B'+C)$

Clear selection

You're editing your response. Sharing this URL allows others to also edit your response.

FILL OUT A NEW RESPONSE


https://docs.google.com/forms/d/e/1FAIpQLScpDHU5B4B3kky_DevHtpVOb4EKd9Mj-VpDp251009458Q/crm/response?edid=2/

8 / 14

7/14



 - 3 Consider the following 4x1 MUX. Here I0-I3 are the input bits and S0-S1 are the two select bits. Which Boolean function does it implement? 1 point



- ☐ $A'B' + C$
☐ ABC
☒ $AB + C$
☐ 1

Clear selection

- 4 Which one of the following is an advantage of an asynchronous counter when compared to a synchronous counter? 1 point

- ☐ Less timing delay
☒ Easier to implement
☐ Requires fewer logic elements
☐ More reliable


Clear selection

☐ A - 00, B - 11, C - 10, D - 01

☐ A - 01, B - 10, C - 11, D - 00

5

 Consider the following circuit. If the frequency of the input clock pulse is 1024Hz, then what will be the frequency of the signal represented by QC? 1 point



☒ 128Hz

☐ 512Hz

☐ 2048Hz

☐ 64Hz

You're editing your response. Sharing this URL allows others to also edit your response.

FILL OUT A NEW RESPONSE

https://docs.google.com/forms/d/e/1FAIpQLScpOHJ5B4B3kky_DnxHtpvCb4EKd9Kj-VIPDp251009458Q/formResponse?edid=2_ABaOnudRK5Tx... 5/14

7/14/2021

Jan 2021 CSE 206 Quiz Section A

6

Which one below is not a valid state of a 5-bit twisted-ring counter?

6 / 14



☐ 11100

☒ 01110

☐ 00111

☐ 11110

Clear selection

7

You are given two 2-bit synchronous up counters. You have to design a 4-bit up counter using them. Which one of the following is true? 1 point

☐ It cannot be done

☐ It can be done using extra logic gates

☐ It can be done using another 2-bit up counter

☒ Both (b) and (c)

8

Which of the following is not a correct property of a moore machine? 1 point

☐ Asynchronous output and state generation

☐ Output depends only upon present state

☐ They react slower to inputs (One clock cycle later)

☒ If input changes, output does change

Clear selection

You're editing your response. Sharing this URL allows others to also edit your response.

FILL OUT A NEW RESPONSE

https://docs.google.com/forms/d/e/1FAIpQLScpOHJ5B4B3kky_DnxHtpvCb4EKd9Kj-VIPDp251009458Q/formResponse?edid=2_ABaOnudRK5Tx... 6/14

7/14/2021

Jan 2021 CSE 206 Quiz Section A

Consider the following circuit of priority encoder. What is the correct priority order of the input lines? 1 point

☒ All of the above Boolean functions can be implemented using a single 4x1 MUX

You're editing your response. Sharing this URL allows others to also edit your response.

FILL OUT A NEW RESPONSE

https://docs.google.com/forms/d/e/1FAIpQLScpDHJ5B4B3kfy_DvHhpVOb4EKx9Mj-VpDp251009458Q/formResponse?edid=2_AbaOnuRK5Tx... 3/14

7/14/2021

Jan 2021 CSE 206 Quiz Section A

9 Which of the following Boolean functions is not equal to $F(x,y,z) = \Sigma(1,2,5,7)$? 1 point

- ☐ $y'z + x'yz' + xz$
- ☐ $x'yz' + x'y'z + xy'z + xyz$
- ☒ $y'z + x'y + xyz$
- ☐ $y'z + x'yz' + xyz$

Clear selection

10 The SOP form for the function $f(A,B,C,D) = \Sigma m(0,2,4,8,10,14)$ is 1 point

- ☐ $BD' + ACD' + A'C'D'$
- ☐ $B'D + ACD' + A'C'D'$
- ☒ $B'D' + ACD' + A'C'D'$
- ☐ $B'D' + ACD' + A'C'D'$

Clear selection

4 / 14



You're editing your response. Sharing this URL allows others to also edit your response.

FILL OUT A NEW RESPONSE

https://docs.google.com/forms/d/e/1FAIpQLScpDHJ5B4B3kfy_DvHhpVOb4EKx9Mj-VpDp251009458Q/formResponse?edid=2_AbaOnuRK5Tx... 4/14

7/14/2021


Jan 2021 CSE 206 Quiz Section A

11 Which one of the following is a race free state assignment for the following flow table? 1 point

	00	01	11	10
A	(A),0	D,0	B,-	(A),0
B	A,-	-	C,-	-
C	A,-	(C),1	(C),1	(C),1
D	A,0	(D),0	(D),0	C,-

- ☐ A - 00, B - 01, C - 10, D - 11
- ☒ A - 01, B - 00, C - 10, D - 11
- ☐ A - 00, B - 11, C - 10, D - 01
- ☐ A - 01, B - 10, C - 11, D - 00

 Consider the following circuit. If the frequency of the input clock pulse is 1024Hz, then what will be the frequency of the signal represented by QC? 1 point




- ☐ Any boolean function can be implemented using 4x1 multiplexers only.
- ☐ Any boolean function can be implemented using 2x1 multiplexers only.
- ☐ Any boolean function can be implemented using NOR gates only.
- ☒ All of the above statements are true.

Clear selection

12

Which boolean function does the following circuit implement?

1 point

 

- ☐ $x'y$
- ☒ xy
- ☐ 0
- ☐ $x + y'$

Clear selection

3 / 14



You're editing your response. Sharing this URL allows others to also edit your response.

FILL OUT A NEW RESPONSE

https://docs.google.com/forms/d/e/1FAIpQL5qzOHU5B4B3kky_DwHtpVOb4EKd8Mj-VpDp251009458Q/form/Response?edit2=2_AbaOnudRK5Tx... 2/14

7/14/2021

Jan 2021 CSE 206 Quiz Section A

13

If you want to mimic the behavior of a 35-state ring counter using a module-35 counter, which of the below additional components would suffice?

1 point

- ☐ 4-to-16 decoder
- ☐ 5-to-32 decoder
- ☐ 3-to-8 decoder
- ☒ 6-to-64 decoder

Clear selection

14

Which propagation delay mainly limits the speed of a ripple counter?

1 point

- ☐ All flip-flops and gates
- ☐ Only circuit gates
- ☒ Each flip-flop
- ☐ None of the above

Clear selection

15

Which of the following boolean function cannot be implemented using a single 4x1 MUX only(not even using any extra NOT gate)?

1 point

- ☐ $F(a,b,c) = a \text{ XOR } b$
- ☐ $F(a,b,c) = ab'c$
- ☐ $F(a,b,c) = ab + c'$
- ☒ All of the above Boolean functions can be implemented using a single 4x1 MUX

You're editing your response. Sharing this URL allows others to also edit your response.

FILL OUT A NEW RESPONSE



7/14/2021

Jan 2021 CSE 206 Quiz Section A

Jan 2021 CSE 206 Quiz Section A

Questions

16

You are to convert a decade counter to a Grey counter. What is the minimum number of logic gates required to make the conversion?

1 point

- ☐ 2
- ☒ 3
- ☐ 4
- ☐ 5

Clear selection

17

How many OR gates are required to implement a Decimal to BCD encoder?

1 point

- ☐ 5
- ☐ 2
- ☒ 4
- ☐ 3

Clear selection

You're editing your response. Sharing this URL allows others to also edit your response.

FILL OUT A NEW RESPONSE

https://docs.google.com/forms/d/e/1FAIpQLScpDHJ5B4B3lky_DruHtpVOb4EKc9Mj-VpDp251009458Q/formResponse?ed2=2_AbaCrudRK5Tx... 1/14

7/14/2021

Jan 2021 CSE 206 Quiz Section A

18

Which of the following statement is false (if any)?


1 point

- ☐ Any boolean function can be implemented using 4x1 multiplexers only.
- ☐ Any boolean function can be implemented using 2x1 multiplexers only.
- ☐ Any boolean function can be implemented using NOR gates only.
- ☒ All of the above statements are true.

Clear selection

Which boolean function does the following circuit implement?

1 point

 

19 A positive edge-triggered D flip-flop will store a 1 when 1 point

- ☒ The D input is HIGH and the clock transitions from LOW to HIGH
- ☐ The D input is HIGH and the clock transitions from HIGH to LOW
- ☐ The D input is HIGH and the clock is LOW
- ☐ The D input is HIGH and the clock is HIGH

Clear selection

20 The inputs of a one bit comparator are A and B and the output is Y. Which of the following equations will give the right output for $A = B$? 1 point

- ☐ $Y = AB' + AB$
- ☐ $Y = A'B' + A'B$
- ☐ $Y = AB' + A'B$
- ☒ $Y = A'B' + AB$

Clear selection

You're editing your response. Sharing this URL allows others to also edit your response.


FILL OUT A NEW RESPONSE

https://docs.google.com/forms/d/e/1FAIpQLScpQHJ5B4B3xkky_DrxHhpVO64EKx9Mj-VfPDp251009458Q/form/Response?edit2=2_ABaCnuDRK5... 12/14

7/14/2021

Jan 2021 CSE 206 Quiz Section A

 21 Consider the following 3x8 Decoder. Here x,y,z are the decoder inputs and o0 to o7 are the eight decoder output lines. Suppose you want to implement the boolean function $F(x,y,z) = xy + yz$. Which output lines need to be ORed to implement the desired function? 1 point



- ☐ o0, o1, o2, o4, o5
- ☒ o3, o6, o7
- ☐ o2, o5, o6
- ☐ o2, o5, o3, o6

Clear selection

22 The logic circuits whose outputs at any instant of time depends not only on the present input but also on the past outputs are called 1 point

- ☐ Flip-flops
- ☐ Combinational circuits
- ☐ Latches
- ☒ Sequential circuits

Clear selection

You're editing your response. Sharing this URL allows others to also edit your response.

FILL OUT A NEW RESPONSE

https://docs.google.com/forms/d/e/1FAIpQLScpQHJ5B4B3xkky_DrxHhpVO64EKx9Mj-VfPDp251009458Q/form/Response?edit2=2_ABaCnuDRK5... 13 / 14

7/14/2021

Jan 2021 CSE 206 Quiz Section A

Never submit passwords through Google Forms.

This form was created inside of Department of Computer Science and Engineering, BUET. [Report Abuse](#)


Google Forms

7/14/2021

Jan 2021 CSE 206 Quiz Section A

23

 In the following Merger Diagram which of the following sets of states is a minimal closed covering. 1 point



- ☐ ABDF, CE
- ☒ ADF, BCE
- ☐ ADF, BDE
- ☐ ABD, CEF

Clear selection

24

Which of the following is not correct for an Encoder? 1 point

- ☐ The number of inputs accepted by an encoder is 2^n
- ☐ The output lines for an encoder is n
- ☒ AND gate is the basic logic element used in it
- ☐ It performs the reverse operation of a Decoder

Clear selection

You're editing your response. Sharing this URL allows others to also edit your response.

FILL OUT A NEW RESPONSE

7/14/2021

Jan 2021 CSE 206 Quiz Section A

25

It should be kept in mind that don't care terms should be used along with the terms that are present in 1 point

- ☐ Latches
- ☐ Minterms
- ☒ K-Map
- ☐ Expressions

Clear selection

26

A positive edge-triggered D flip-flop will store a 1 when 1 point

- ☒ The D input is HIGH and the clock transitions from LOW to HIGH
- ☐ The D input is HIGH and the clock transitions from HIGH to LOW
- ☐ The D input is HIGH and the clock is LOW
- ☐ The D input is HIGH and the clock is HIGH

Clear selection

The inputs of a one bit comparator are A and B and the output is Y. Which of the following equations will give the right output for $A = B$? 1 point


- ☐ $Y = \Delta R' + \Delta R$

12 / 14



27

 Consider the following 4x1 MUX. Here I0-I3 are the inputs and S0,S1 are the selection bits. 'Out' is the output line. Suppose you want to implement the Boolean function $AB+BC$. What inputs should you give to the input lines? 1 point



- ☒ I0 = 0, I1 = C, I2 = 0, I3 = 1
- ☐ I0 = 1, I1 = C, I2 = C, I3 = 1
- ☐ I0 = 0, I2 = C, I2 = 0, I3 = C
- ☐ It is not possible to implement $AB+BC$ using a single 4x1 MUX.

Clear selection

28

A basic S-R flip-flop can be constructed by cross-coupling of which logic gates? 1 point

- ☐ XOR or XNOR gates
- ☒ NOR or NAND gates
- ☐ AND or NOR gates
- ☐ AND or OR gates

Clear selection

You're editing your response. Sharing this URL allows others to also edit your response.

FILL OUT A NEW RESPONSE

https://docs.google.com/forms/d/e/1FAIpQLScpOHJ5B4B3kEky_DexHhpVOb4EKd9Mj-VfPdp251009458Q/formResponse?edit=2_AbaOnudRKSTx... 9/14

29

A full adder circuit is given with three inputs x, y and z. You have to design a full subtractor using this full adder circuits with x denoting minuend, y denoting subtrahend and z is the previous borrow. It can be done by: 1 point

- ☐ None of the above
- ☒ Complementing the input x to the circuit of carry out of the full adder
- ☐ Complementing the input y to the circuit of carry out of the full adder
- ☐ Complementing the input z to the circuit of carry out of the full adder

Clear selection

10 / 14



30

Which of the following input transition is valid for inputs X1X2X3 of a fundamental mode circuit? 1 point

- ☒ 010 → 110
- ☐ 011 → 100
- ☐ 000 → 011
- ☐ 100 → 010

Clear selection

When overflow occurs in a 20-bit ripple counter, how many transient states does it transition through? 1 point

- ☐ 2^{19}
- ☐ 20